DI-39 Design Idea TOPSwitch-GX



13 W, Universal Input DVD Supply with 70 mW No-load

Application	Device	Power Output	Input Voltage	Output Voltage	Тороlоду	
DVD	TOP244PN	13 W cont, 17 W pk	85 – 265 VAC	3.3 V, 5 V, 12 V, -12 V	Flyback	

Design Highlights

- High efficiency multi-ouptut flyback (77% minimum)
- Topology scalable to higher powers
- Excellent cross-regulation
- Excellent input no-load consumption <70 mW input
- 132 kHz switching frequency allows smaller transformer
- Frequency jitter eliminates common-mode EMI choke
- >10 dB margin against CISPR22-B conducted EMI with artificial hand grounding

Operation

The TOPSwitch-GX uses current mode feedback to achieve excellent no-load standby. Components C16, R1 and Q2 provide a constant current powering the TOPSwitch-GX CONTROL pin. Resistor R2 feeds the remainder of Q2 current to the M pin, reducing TOPSwitch-GX current limit with increased current.

Resistor R11 sets the maximum current limit of the device. Components R6, Q1 and C13 implement slope compensation. The supply operates at full frequency at high and medium power and reduces frequency at light loads. Components D9 and C10 rectify and filter the bias voltage. TOPSwitch-GX frequency jitter allows conducted EMI compliance without a common-mode choke, using only capacitors C1, C4 and inductor L1 as an EMI filter.

Components D5 and C2 form a capacitor clamp circuit absorbing leakage inductance energy during normal operation. Zener VR1 clamps the voltage to a safe level during abnormal and transient conditions. After clamping, reverse current flows through D5, recovering some of the energy. Resistor R5 limits the reverse current and, with R7, improves EMI by limiting the ringing on the drain. Continuous mode operation allows reduced primary and secondary peak currents, optimizing cross regulation and load regulation by minimizing leakage inductance induced voltage shifts.

Resistors R15 and R16 share the feedback from the 3.3 V and 5 V outputs for good cross-regulation.



Key Design Points

- Use of foil for the 3.3 V and 5 V windings also helps to optimize cross-regulation.
- Optional capacitor C7 is the "soft-finish" capacitor and prevents overshoot on startup.
- Compact layout for components D7, D10, D11, C11, C12, C15 will improve cross-regulation and efficiency. Compact layout for L2, L3, L4, C17, C18, and C20 will achieve best output ripple.
- Figure 2 shows conducted EMI at 230 VAC full load, with output "Artificial Hand" grounding. Floating output return gives lower results.
- Table 2 shows the cross regulation of the supply over load for both 115 VAC and 230 VAC.



Figure 2. EMI at 230 VAC Full Load with "Artificial Hand" Grounding of Output.

Transformer Parameters EEL25 Himag MZ4 EEL25.4, Taiwan ALG of **Core Material** 344 nH/t² Bobbin EEL25 14 pin, Vertical Shield: 32T × 2 × 32 AWG Primary: 64T × 2 × 32 AWG Bias: 10T × 4 × 32 AWG Shield: 2T × 8 × 32 AWG Winding Details +3.3 V: 4T × foil 0.052 × 14 mm +5 V: 1T × foil 0.052 × 14 mm +12 V: 4T × 4 × 32 AWG -12 V: 7T × 4 × 32 AWG Shield (NC-5), tape, Primary (1-4), tape, Bias Winding Order (7-6), tape, Shield (5-NC), tape, +12 V (13-8), (pin numbers) +3.3 V (11,12-9,10), +5 V (9-10,13), tape, -12 V (14-11,12), tape **Primary Inductance** 1.42 mH, ±10% at 132 kHz (pins 1-4, all others öpen) **Primary Resonant** 300 kHz (minimum) Frequency Leakage 30 µH (maximum) Inductance

Table 1. Transformer Parameters. (AWG = American Wire Gauge, NC = No Connection)

Output Voltage (V)	Load Range (%)	Cross Regulation (%)									
		-4	-3	-2	-1	0	1	2	3	4	
3.3	10-100										
5	10-100										
12	10-100										
-12	10-100										

Table 2.Worst Case Cross Regulation at 115 VAC and 230 VAC.

Power Integrations 5245 Hellyer Avenue San Jose, CA 95138, USA. Main: +1 408-414-9200 *Customer Service* Phone: +1-408-414-9665 Fax: +1-408-414-9765 Email: usasales@powerint.com

On the Web www.powerint.com Power Integrations reserves the right to make changes to its products at any time to improve reliability or manufacturability. Power Integrations does not assume any liability arising from the use of any device or circuit described herein. POWER INTEGRATIONS MAKES NO WARRANTY HEREIN AND SPECIFICALLY DISCLAIMS ALL WARRANTIES INCLUDING, WITHOUT LIMITATION, THE IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF THIRD PARTY RIGHTS. The products and applications illustrated herein (transformer construction and circuits external to the products) may be covered by one or more U.S. and foreign patents or potentially by pending U.S. and foreign patent applications assigned to Power Integrations. A complete list of Power Integrations' patents may be found at www.powerint.com. Power Integrations grants its customers a license under certain patent rights as set forth at http://www.powerint.com/ip.htm.

The PI logo, TOPSwitch, TinySwitch, LinkSwitch, DPA-Switch, PeakSwitch, EcoSmart, Clampless, E-Shield, Filterfuse, StackFET, PI Expert and PI FACTS are trademarks of Power Integrations, Inc. Other trademarks are property of their respective companies. ©2002, Power Integrations, Inc.