

DI-26 Design Idea

TOPSwitch-GX

7 W Digital Video Broadcast-Terrestrial (DVB-T) Supply

Application	Device	Power Output	Input Voltage	Output Voltage	Topology
DVB-T	TOP242PN	7 W	195 – 265 VAC	2.5 V / 3.3 V / 6.2 V / 30 V	Flyback

Design Highlights


- Meets CISPR22B/EN55022B conducted EMI limits with output return grounded
- <0.5 W input power at zero load
- 132 kHz operation and programmable current limit allows small, low cost EF16 transformer for 7 W output
- Low component count design occupies 80 × 30 × 16 mm
- Integrated soft-start reduces start-up component stresses

Operation

The TOPSwitch-GX flyback supply provides 4 outputs, delivering 7 W from a 230 VAC ±15% input. The TOP242PN was selected for low cost, the DIP-8 package removing the need for an external heat sink. Resistor R7 programs the internal TOP242PN current limit to 78% of nominal, just above the level needed for full load at low line. This feature allows a more continuous transformer design for better efficiency and cross-regulation, without requiring a larger core size.

Resistor R12, C10 and L2 filter conducted EMI; R12 is a flame-proof fusible type, also functioning as a fuse. For lower cost, if the supply does not have to meet conducted EMI with the output connected to earth ground, the common mode choke can be replaced with a π filter. A Zener clamp (D11 and VR1) was selected over an RCD clamp to minimize zero load consumption. Secondary side feedback is taken from the 3.3 V ±5% output since this has the tightest tolerance requirement. The 2.5 V ±5% output is derived directly from the 3.3 V output using D4. A 60 V Schottky was selected for D1, since the slightly higher forward drop centers the 6.2 V and 30 V outputs.

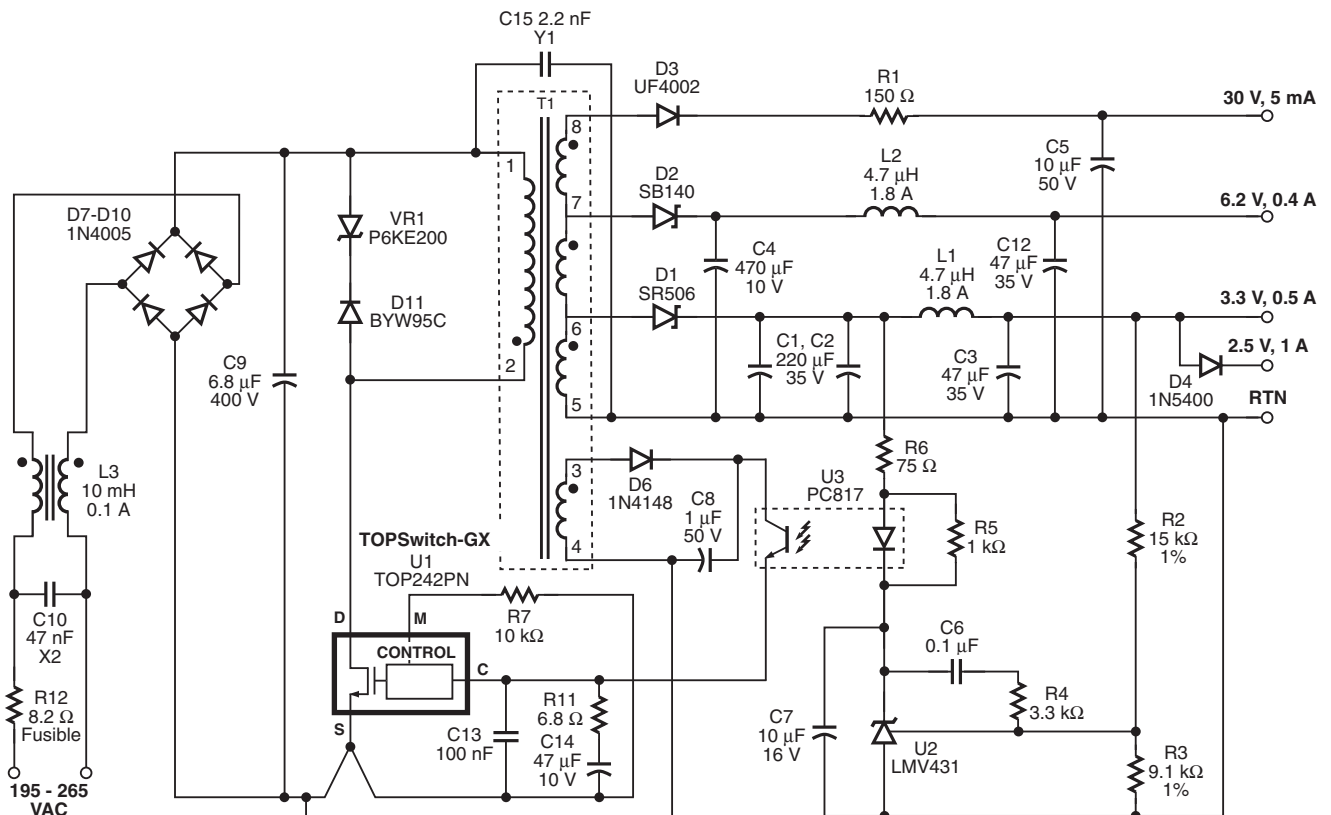Post-filters (L1/C3, L2/C12 and R1/C5) reduce output noise and ripple to <±1% of the respective output voltage. A soft-finish capacitor (C7) eliminates output turn-on overshoot.



PI-3023-101308

Figure 1. TOPSwitch-GX 7 W Multiple Output Supply for DVB-T.

Key Design Points

- The transformer is designed to operate in continuous mode for tight secondary cross-regulation.
- Safety Y1 capacitor C15 is connected between secondary return and primary DC rail to minimize noise coupling during AC common mode line transients.
- Good layout practices should be followed:
 - Locate C13, R11 and C14 close to U1, with grounds returned to the SOURCE pin.
 - Minimize the primary and secondary loop areas to reduce parasitic leakage inductance, improve EMI and cross-regulation.

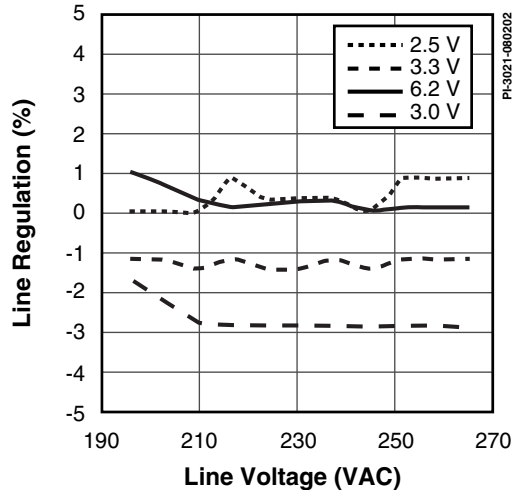


Figure 2. Full Power Line Regulation.

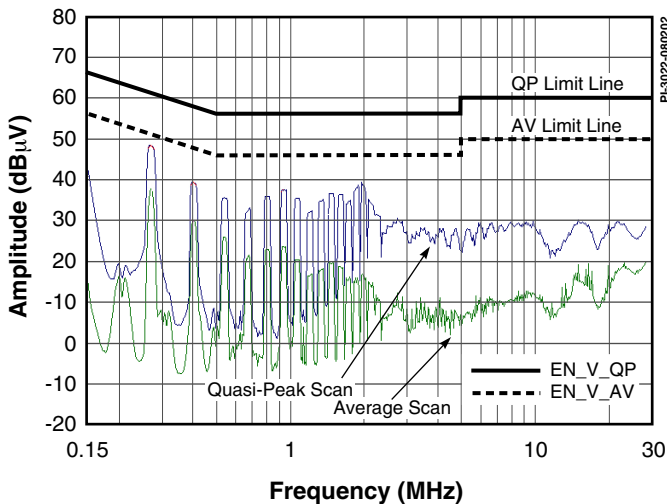


Figure 3. Conducted EMI, 230 VAC, Full Power, Output Earth Grounded.

Transformer Parameters

Core Material	EF16, gapped for 190 nH/t ²
Bobbin	EF16-8 pin
Winding Details	Primary: 105T, 35 AWG Bias: 17T, 35 AWG 3.3 V Secondary: 4T, 4 × 26 AWG T.I.W. 6.2 V Secondary: 3T, 26 AWG T.I.W. 30 V Secondary: 29T, 30 AWG T.I.W.
Winding Order	Primary (1–2), tape, Bias (3–4), tape, 3.3 V (5–6), 5 V (6–7), 30 V (7–8)
Inductance	Primary: 2.1 mH ±10% Leakage: 50 µH (maximum)
Primary Resonant Frequency	650 kHz (minimum)

Table 1. Transformer Parameters. (AWG = American Wire Gauge, T.I.W. = Triple Insulated Wire)

Voltage (V)	Load Range (%)	Regulation (%)																		
		-10	-7	-4	-3	-2	-1	0	1	2	3	4	7							
3.3	10-100																			
5	10-100																			
30	10-100																			
	100																			

Table 2. Worst Case Output Cross-Regulation – All Outputs Taken from Minimum to Maximum Load.

Power Integrations
5245 Hellyer Avenue
San Jose, CA 95138, USA.
Main: +1 408-414-9200
Customer Service
Phone: +1-408-414-9665
Fax: +1-408-414-9765
Email: usasales@powerint.com

On the Web
www.powerint.com

Power Integrations reserves the right to make changes to its products at any time to improve reliability or manufacturability. Power Integrations does not assume any liability arising from the use of any device or circuit described herein. POWER INTEGRATIONS MAKES NO WARRANTY HEREIN AND SPECIFICALLY DISCLAIMS ALL WARRANTIES INCLUDING, WITHOUT LIMITATION, THE IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF THIRD PARTY RIGHTS. The products and applications illustrated herein (transformer construction and circuits external to the products) may be covered by one or more U.S. and foreign patents or potentially by pending U.S. and foreign patent applications assigned to Power Integrations. A complete list of Power Integrations' patents may be found at www.powerint.com. Power Integrations grants its customers a license under certain patent rights as set forth at <http://www.powerint.com/ip.htm>.

The PI logo, TOPSwitch, TinySwitch, LinkSwitch, DPA-Switch, PeakSwitch, EcoSmart, Clampless, E-Shield, Filterfuse, StackFET, PI Expert and PI FACTS are trademarks of Power Integrations, Inc. Other trademarks are property of their respective companies. ©2002, Power Integrations, Inc.